

UNIVERSITY OF DUBLIN,  
TRINITY COLLEGE



---

COMPUTER ARCHITECTURE I (CS2022)  
PROJECT 2 - MICROCODED INSTRUCTION SET PROCESSOR

---

*Author:*

Edmond O'FLYNN 12304742

*Lecturer:*

Dr. Michael MANZKE

April 5, 2016

# Contents

<b>1</b>	<b>VHDL Component Source Code</b>	<b>1</b>
1.1	ALU Unit . . . . .	1
1.2	Control Address Register . . . . .	2
1.3	Control Memory . . . . .	3
1.4	Datapath . . . . .	9
1.5	Decoder 4-9 Bit . . . . .	11
1.6	Extended Programme Counter . . . . .	12
1.7	Full Adder . . . . .	12
1.8	Function Unit . . . . .	12
1.9	Instruction Register . . . . .	14
1.10	Logic Circuit A-B . . . . .	14
1.11	Logic Circuit B . . . . .	15
1.12	Memory Module . . . . .	17
1.13	Microprogramme Controller . . . . .	21
1.14	Mux 2-1 Bit . . . . .	24
1.15	Mux 2-8 Bit . . . . .	24
1.16	Mux 2-16 Bit . . . . .	25
1.17	Mux 3-1 Bit . . . . .	25
1.18	Mux 8-1 Bit . . . . .	26
1.19	Mux 9-16 Bit . . . . .	26
1.20	Programme Counter . . . . .	27
1.21	Project 2 Top Level . . . . .	27
1.22	Register . . . . .	29
1.23	Register File . . . . .	29
1.24	Ripple Adder . . . . .	33
1.25	Shifter . . . . .	36
1.26	Zero Fill . . . . .	39
<b>2</b>	<b>Component Test Benches</b>	<b>40</b>
2.1	Control Address Register . . . . .	40
2.2	Control Memory . . . . .	41
2.3	Decoder 4-9 bit . . . . .	42
2.4	Extended Programme Counter . . . . .	45
2.5	Instruction Register . . . . .	46
2.6	Memory Module . . . . .	47
2.7	Mux 2-8 Bit . . . . .	48
2.8	Mux 8-1 Bit . . . . .	49
2.9	Mux 9-16 Bit . . . . .	51
2.10	Programme Counter . . . . .	53
2.11	Project 2 Top Level . . . . .	55
2.12	Register File . . . . .	56
2.13	Zero Fill . . . . .	58
<b>3</b>	<b>Results of Test Benches</b>	<b>60</b>
3.1	Control Address Register . . . . .	62
3.2	Control Memory . . . . .	62
3.3	Decoder 4-9 bit . . . . .	62
3.4	Extended Programme Counter . . . . .	62
3.5	Instruction Register . . . . .	63
3.6	Memory Module . . . . .	63
3.7	Mux 2-1 Bit . . . . .	63

3.8	Mux 8-1 Bit . . . . .	63
3.9	Mux 9-16 Bit . . . . .	63
3.10	Programme Counter . . . . .	64
3.11	Project 2 Top Level . . . . .	64
3.12	Register File . . . . .	64
3.13	Zero Fill . . . . .	64

# 1 VHDL Component Source Code

## 1.1 ALU Unit

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity alu_unit is
    Port(
        a_in, b_in : in STD_LOGIC_VECTOR(15 downto 0);
        G_select : in STD_LOGIC_VECTOR(3 downto 0);
        V, C : out STD_LOGIC; -- flags
        G : out STD_LOGIC_VECTOR(15 downto 0)
    );

end alu_unit;

architecture Behavioral of alu_unit is

    --components in ALU
    --ripple adder
    Component RippleAdder
        Port(
            A, B : in STD_LOGIC_VECTOR(15 downto 0);
            Cin : in STD_LOGIC;
            Cout, V_out : out STD_LOGIC;
            G_out : out STD_LOGIC_VECTOR(15 downto 0)
        );
    End Component;
    --a b logic for and or xor not
    Component logic_circuit_a_b
        Port(
            a_logic_in, b_logic_in : in STD_LOGIC_VECTOR(15 downto 0);
            select_in : in STD_LOGIC_VECTOR(1 downto 0);
            logic_output_a_b : out STD_LOGIC_VECTOR(15 downto 0)
        );
    End Component;
    --b logic circuit
    Component logic_circuit_b
        Port(
            B : in STD_LOGIC_VECTOR(15 downto 0);
            S_in : in STD_LOGIC_VECTOR(1 downto 0);
            Y_out : out STD_LOGIC_VECTOR(15 downto 0)
        );
    End Component;
    --2-1 mux
    Component Mux2to16
        Port(
            In0, In1 : in STD_LOGIC_VECTOR(15 downto 0);
            s : in STD_LOGIC;
            Z : out STD_LOGIC_VECTOR(15 downto 0)
        );
    End Component;

    signal logic_out, logic_output_a_b, ripple_out : STD_LOGIC_VECTOR(15 downto 0);
```

```

begin
    --instantiation of components
    r_adder: RippleAdder PORT MAP(
        A => a_in,
        B => b_in,
        Cin => G_select(0),
        Cout => C,
        V_out => V,
        G_out => ripple_out
    );

    logic_circuit_a_b00: logic_circuit_a_b PORT MAP(
        a_logic_in => a_in,
        b_logic_in => b_in,
        select_in => G_select(2 downto 1),
        logic_output_a_b => logic_output_a_b
    );

    logic_circuit_b00 : logic_circuit_b PORT MAP(
        B => b_in,
        S_in => G_select(2 downto 1),
        Y_out => logic_out
    );

    mux_2_1600: Mux2to16 PORT MAP(
        In0 => ripple_out,
        In1 => logic_output_a_b,
        s => G_select(3),
        Z => G
    );

end Behavioral;

```

## 1.2 Control Address Register

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ControlAddressRegister is
    Port( car_in : in STD_LOGIC_VECTOR(7 downto 0);
          s_car, reset : in STD_LOGIC;
          car_out : out STD_LOGIC_VECTOR(7 downto 0)
        );
end ControlAddressRegister;

architecture Behavioral of ControlAddressRegister is

begin
    process(reset, car_in)
        variable curr_car : STD_LOGIC_VECTOR(7 downto 0);
        variable temp_curr_car : integer;
        variable temp_inc_car : STD_LOGIC_VECTOR(7 downto 0);
    end process

```

```

begin
    if(reset = '1') then curr_car := x"CO";
    elsif(s_car = '1') then curr_car := car_in;
    elsif(s_car = '0') then
        temp_curr_car := conv_integer(curr_car);
        temp_curr_car := temp_curr_car + conv_integer(1);
        temp_inc_car := conv_std_logic_vector(temp_curr_car, 8);
        curr_car := temp_inc_car;
    end if;
    car_out <= curr_car after 20ns;
end process;
end Behavioral;

```

### 1.3 Control Memory

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ControlMemory is
    Port( in_car : in STD_LOGIC_VECTOR(7 downto 0);
          MW, MM, RW, MD, MB, TB, TA, TD, PL, PI, IL, MC : out STD_LOGIC;
          FS_cm : out STD_LOGIC_VECTOR(4 downto 0);
          MS_cm : out STD_LOGIC_VECTOR(2 downto 0);
          NA : out STD_LOGIC_VECTOR(7 downto 0)
        );
end ControlMemory;

architecture Behavioral of ControlMemory is
    --instantiate an array for each given memory allocation
    type mem_array is array(0 to 255) of STD_LOGIC_VECTOR(27 downto 0);

begin
    memory_m : process(in_car)
        variable ControlMemory : mem_array := (
            --Module 0
            x"C020304", --0 start of intermediate value in register
            x"C020304", --1 immediate value in register
            x"C020304", --2 immediate value in register
            x"C020304", --3 immediate value in register
            x"C020304", --4 immediate value in register
            x"C020304", --5 immediate value in register
            x"C020304", --6 immediate value in register
            x"C020304", --7 end of immediate value in register
            x"C020224", --8 ADI -> add the immediate operand
            x"C02000C", --9 LDR -> load to register
            x"C020001", --A STR -> store in register
            x"C020014", --B INC -> increment the register's value by 1
            x"C0200E4", --C NOT -> compliment
            x"C020024", --D ADD -> add values from source and destination
            x"1228002", --E B -> branch unconditionally
            x"0000000", --F

```

```

--Module 1
x"0000000", --0
x"0000000", --1
x"C020000", --2
x"C020024", --3 ADD -> add values from source and destination
x"169A002", --4 BXX -> branch conditionally to area
x"C020024", --5 ADD -> add values from source and destination
x"C020024", --6 ADD -> add values from source and destination
x"C020024", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F

```

```

--Module 2
x"0000000", --0
x"0000000", --1
x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F

```

```

--Module 3
x"0000000", --0
x"0000000", --1
x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F

```

```

--Module 4

```

```
x"0000000", --0
x"0000000", --1
x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F
```

```
--Module 5
```

```
x"0000000", --0
x"0000000", --1
x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F
```

```
--Module 6
```

```
x"0000000", --0
x"0000000", --1
x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F
```

```
--Module 7
```

```
x"0000000", --0
```



```
x"0000000", --1
x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F
```

```
--Module 8
```

```
x"0000000", --0
x"0000000", --1
x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F
```

```
--Module 9
```

```
x"0000000", --0
x"0000000", --1
x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F
```

```
--Module A
```

```
x"0000000", --0
x"0000000", --1
```

```

x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F

--Module B
x"0000000", --0
x"0000000", --1
x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F

--Module C
x"C10C002", --0 IF fetching
x"0030000", --1 Exit signal
x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F

--Module D
x"0000000", --0
x"0000000", --1
x"0000000", --2

```

```

x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F

--Module E
x"0000000", --0
x"0000000", --1
x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000", --F

--Module F
x"0000000", --0
x"0000000", --1
x"0000000", --2
x"0000000", --3
x"0000000", --4
x"0000000", --5
x"0000000", --6
x"0000000", --7
x"0000000", --8
x"0000000", --9
x"0000000", --A
x"0000000", --B
x"0000000", --C
x"0000000", --D
x"0000000", --E
x"0000000" --F
);

variable addr : integer;
variable control_out : STD_LOGIC_VECTOR(27 downto 0);

begin

```

```

addr := conv_integer(in_car);
control_out := ControlMemory(addr);
MW <= control_out(0);
MM <= control_out(1);
RW <= control_out(2);
MD <= control_out(3);
FS_cm <= control_out(8 downto 4);
MB <= control_out(9);

TB <= control_out(10);
TA <= control_out(11);
TD <= control_out(12);
PL <= control_out(13);
PI <= control_out(14);
IL <= control_out(15);
MC <= control_out(16);
MS_cm <= control_out(19 downto 17);
NA <= control_out(27 downto 20);
end process;

end Behavioral;

```

## 1.4 Datapath

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Datapath is
    Port( data_in, pc_in : in STD_LOGIC_VECTOR(15 downto 0);
          control_word : in STD_LOGIC_VECTOR(17 downto 0);
          clk_sig, TD, TA, TB : in STD_LOGIC;
          data_out, addr_out : out STD_LOGIC_VECTOR(15 downto 0);
          status_out : out STD_LOGIC_VECTOR(3 downto 0)
        );
end Datapath;

architecture Behavioral of Datapath is

    component RegFile
        Port( des_d, add_a, add_b : in STD_LOGIC_VECTOR(3 downto 0);
              Clk, load_in : in STD_LOGIC;
              data : in STD_LOGIC_VECTOR(15 downto 0);
              out_data_a, out_data_b : out STD_LOGIC_VECTOR(15 downto 0)
            );
    end component;

    component Mux2to16
        Port( In0, In1 : in STD_LOGIC_VECTOR(15 downto 0);
              s : in STD_LOGIC;
              Z : out STD_LOGIC_VECTOR(15 downto 0)
            );
    end component;

    component ZeroFill
        Port( SB_in : in STD_LOGIC_VECTOR(2 downto 0);

```

```

        zero_fill_out : out STD_LOGIC_VECTOR(15 downto 0)
    );
end component;

component FunctionUnit
    Port( FunctionSelect : in STD_LOGIC_VECTOR(4 downto 0);
          a_in, b_in : in STD_LOGIC_VECTOR(15 downto 0);
          N_fu, Z_fu, V_fu, C_fu : out STD_LOGIC;
          F : out STD_LOGIC_VECTOR(15 downto 0)
    );
end component;

signal mux_b_out, mux_d_out, mux_m_out, reg_file_out_a, reg_file_out_b, func_unit_out,
        zero_fill_out, pc_sig : STD_LOGIC_VECTOR(15 downto 0);
signal dest_d, addr_a, addr_b, status_bits : STD_LOGIC_VECTOR(3 downto 0);

begin

mux_b : Mux2to16 PORT MAP(
    In0 => reg_file_out_b,
    In1 => zero_fill_out,
    s => control_word(8),
    Z => mux_b_out
);

mux_d : Mux2to16 PORT MAP(
    In0 => func_unit_out,
    In1 => data_in,
    s => control_word(2),
    Z => mux_d_out
);

pc_sig <= pc_in;

mux_m : Mux2to16 PORT MAP(
    In0 => reg_file_out_a,
    In1 => pc_sig,
    s => control_word(0),
    Z => mux_m_out
);

dest_d <= TD & control_word(17 downto 15);
addr_a <= TA & control_word(14 downto 12);
addr_b <= TB & control_word(11 downto 9);

zero_fill : ZeroFill PORT MAP(
    SB_in => control_word(11 downto 9),
    zero_fill_out => zero_fill_out
);

reg_file : RegFile PORT MAP(
    des_d => dest_d,
    add_a => addr_a,
    add_b => addr_b,
    Clk => clk_sig,

```

```

    load_in => control_word(1),
    data => mux_d_out,
    out_data_a => reg_file_out_a,
    out_data_b => reg_file_out_b
);

data_out <= mux_b_out;
addr_out <= mux_m_out;

func_unit : FunctionUnit PORT MAP(
    FunctionSelect => control_word(7 downto 3),
    a_in => reg_file_out_a,
    b_in => mux_b_out,
    N_fu => status_bits(1),
    Z_fu => status_bits(0),
    V_fu => status_bits(3),
    C_fu => status_bits(2),
    F => func_unit_out
);

status_out <= status_bits;

end Behavioral;

```

## 1.5 Decoder 4-9 Bit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decoder4to9 is
    Port( A0, A1, A2, A3 : in STD_LOGIC;
          Q0, Q1, Q2, Q3, Q4, Q5, Q6, Q7, Q8 : out STD_LOGIC
    );
end Decoder4to9;

architecture Behavioral of Decoder4to9 is

begin
    Q0 <= ((not A0) and (not A1) and (not A2) and (not A3)) after 1ns; --0000
    Q1 <= ((A0) and (not A1) and (not A2) and (not A3)) after 1ns; --1000
    Q2 <= ((not A0) and (A1) and (not A2) and (not A3)) after 1ns; --0100
    Q3 <= ((A0) and (A1) and (not A2) and (not A3)) after 1ns; --1100
    Q4 <= ((not A0) and (not A1) and (A2) and (not A3)) after 1ns; --0010
    Q5 <= ((A0) and (not A1) and (A2) and (not A3)) after 1ns; --1010
    Q6 <= ((not A0) and (A1) and (A2) and (not A3)) after 1ns; --0110
    Q7 <= ((A0) and (A1) and (A2) and (not A3)) after 1ns; --1110
    Q8 <= ((not A0) and (not A1) and (not A2) and (A3)) after 1ns; --0001

end Behavioral;

```

## 1.6 Extended Programme Counter

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ExtendedProgrammeCounter is
    Port( SR_SB : in STD_LOGIC_VECTOR(5 downto 0);
          ExtendedProgrammeCounter : out STD_LOGIC_VECTOR(15 downto 0)
        );
end ExtendedProgrammeCounter;

architecture Behavioral of ExtendedProgrammeCounter is
    signal extended_signal : STD_LOGIC_VECTOR(15 downto 0);
begin
    extended_signal(5 downto 0) <= SR_SB;
    extended_signal(15 downto 6) <= "0000000000" when SR_SB(5) = '0' else "1111111111";
    ExtendedProgrammeCounter <= extended_signal;

end Behavioral;
```

## 1.7 Full Adder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity FullAdder is
    Port(
        X, Y, Cin : in STD_LOGIC;
        Cout, S : out STD_LOGIC
    );
end FullAdder;

architecture Behavioral of FullAdder is
    signal S0, S1, S2 : STD_LOGIC;
begin
    S0 <= (X xor Y) after 1ns;
    S1 <= (Cin and S0) after 1ns;
    S2 <= (X and Y) after 1ns;
    S <= (S0 xor Cin) after 1ns;
    Cout <= (S1 or S2) after 1ns;

end Behavioral;
```

## 1.8 Function Unit

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity FunctionUnit is
    Port(
        FunctionSelect : in STD_LOGIC_VECTOR(4 downto 0); -- 5 input
        a_in, b_in : in STD_LOGIC_VECTOR(15 downto 0);
        N_fu, Z_fu, V_fu, C_fu : out STD_LOGIC;
        F : out STD_LOGIC_VECTOR(15 downto 0)
    );
```

```

end FunctionUnit;

architecture Behavioral of FunctionUnit is

    --2 to 1 mux
    Component Mux2to16
    Port(
        In0, In1 : in STD_LOGIC_VECTOR(15 downto 0);
        s : in STD_LOGIC;
        Z : out STD_LOGIC_VECTOR(15 downto 0)
    );
End Component;

    --shifter
    Component shifter
    Port(
        B : in STD_LOGIC_VECTOR(15 downto 0);
        S : in STD_LOGIC_VECTOR(1 downto 0);
        IL, IR : in STD_LOGIC;
        H : out STD_LOGIC_VECTOR(15 downto 0)
    );
End Component;

    --alu
    Component alu_unit
    Port(
        a_in, b_in : in STD_LOGIC_VECTOR(15 downto 0);
        G_select : in STD_LOGIC_VECTOR(3 downto 0);
        V, C : out STD_LOGIC; -- flags
        G : out STD_LOGIC_VECTOR(15 downto 0)
    );
End Component;

    signal H_out, ALU_out, mux_out : STD_LOGIC_VECTOR(15 downto 0);

begin

    shifter00: shifter PORT MAP(
        B => b_in,
        S => FunctionSelect(3 downto 2),
        IL => '0',
        IR => '0',
        H => H_out
    );

    mux_2_1600: Mux2to16 PORT MAP(
        In0 => ALU_out,
        In1 => H_out,
        s => FunctionSelect(4),
        z => mux_out
    );

    alu: alu_unit PORT MAP(
        a_in => a_in,
        b_in => b_in,
        G_select => FunctionSelect(3 downto 0),
        V => V_fu,
        C => C_fu,

```



```

    G => ALU_out
);

F <= mux_out;
N_fu <= mux_out(15);
Z_fu <= (mux_out(15) or mux_out(14) or mux_out(13) or mux_out(12) or mux_out(11)
        or mux_out(10) or mux_out(9) or mux_out(8) or mux_out(7) or mux_out(6)
        or mux_out(5) or mux_out(4) or mux_out(3) or mux_out(2) or mux_out(1) or
        mux_out(0));

end Behavioral;

```

## 1.9 Instruction Register

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Instructions is
    Port( IR_in : in STD_LOGIC_VECTOR(15 downto 0);
          IL_in : in STD_LOGIC;
          Opcode : out STD_LOGIC_VECTOR(6 downto 0);
          DR_out, SA_out, SB_out : out STD_LOGIC_VECTOR(2 downto 0)
        );
end Instructions;

architecture Behavioral of Instructions is

begin
    Opcode <= IR_in(15 downto 9) after 1ns when IL_in = '1';
    DR_out <= IR_in(8 downto 6) after 1ns when IL_in = '1';
    SA_out <= IR_in(5 downto 3) after 1ns when IL_in = '1';
    SB_out <= IR_in(2 downto 0) after 1ns when IL_in = '1';

end Behavioral;

```

## 1.10 Logic Circuit A-B

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity logic_circuit_a_b is
    Port(
        a_logic_in, b_logic_in : in STD_LOGIC_VECTOR(15 downto 0);
        select_in : in STD_LOGIC_VECTOR(1 downto 0);
        logic_output_a_b : out STD_LOGIC_VECTOR(15 downto 0)
    );
end logic_circuit_a_b;

architecture Behavioral of logic_circuit_a_b is

begin
    logic_output_a_b <= (a_logic_in and b_logic_in) after 1ns when select_in = "00" else
        (a_logic_in or b_logic_in) after 1ns when select_in = "01" else
        (a_logic_in xor b_logic_in) after 1ns when select_in = "10" else
        (not (a_logic_in)) after 1ns;
end Behavioral;

```

```
end Behavioral;
```

## 1.11 Logic Circuit B

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity logic_circuit_b is
```

```
  Port(
```

```
    B : in STD_LOGIC_VECTOR(15 downto 0);
```

```
    S_in : in STD_LOGIC_VECTOR(1 downto 0);
```

```
    Y_out : out STD_LOGIC_VECTOR(15 downto 0)
```

```
  );
```

```
end logic_circuit_b;
```

```
architecture Behavioral of logic_circuit_b is
```

```
  --mux 2-1 component
```

```
  Component Mux2to1
```

```
  Port(
```

```
    B_i, S0, S1 : in STD_LOGIC;
```

```
    Y_i : out STD_LOGIC
```

```
  );
```

```
  End Component;
```

```
begin
```

```
  mux00: Mux2to1 PORT MAP(
```

```
    B_i => B(0),
```

```
    S0 => S_in(0),
```

```
    S1 => S_in(1),
```

```
    Y_i => Y_out(0)
```

```
  );
```

```
  mux01: Mux2to1 PORT MAP(
```

```
    B_i => B(1),
```

```
    S0 => S_in(0),
```

```
    S1 => S_in(1),
```

```
    Y_i => Y_out(1)
```

```
  );
```

```
  mux02: Mux2to1 PORT MAP(
```

```
    B_i => B(2),
```

```
    S0 => S_in(0),
```

```
    S1 => S_in(1),
```

```
    Y_i => Y_out(2)
```

```
  );
```

```
  mux03: Mux2to1 PORT MAP(
```

```
    B_i => B(3),
```

```
    S0 => S_in(0),
```

```
    S1 => S_in(1),
```

```
    Y_i => Y_out(3)
```

```
  );
```

```

mux04: Mux2to1 PORT MAP(
    B_i => B(4),
    S0 => S_in(0),
    S1 => S_in(1),
    Y_i => Y_out(4)
);

mux05: Mux2to1 PORT MAP(
    B_i => B(5),
    S0 => S_in(0),
    S1 => S_in(1),
    Y_i => Y_out(5)
);

mux06: Mux2to1 PORT MAP(
    B_i => B(6),
    S0 => S_in(0),
    S1 => S_in(1),
    Y_i => Y_out(6)
);

mux07: Mux2to1 PORT MAP(
    B_i => B(7),
    S0 => S_in(0),
    S1 => S_in(1),
    Y_i => Y_out(7)
);

mux08: Mux2to1 PORT MAP(
    B_i => B(8),
    S0 => S_in(0),
    S1 => S_in(1),
    Y_i => Y_out(8)
);

mux09: Mux2to1 PORT MAP(
    B_i => B(9),
    S0 => S_in(0),
    S1 => S_in(1),
    Y_i => Y_out(9)
);

mux10: Mux2to1 PORT MAP(
    B_i => B(10),
    S0 => S_in(0),
    S1 => S_in(1),
    Y_i => Y_out(10)
);

end Behavioral;

```

## 1.12 Memory Module

[illegible]

[illegible]

[illegible]

[illegible]

```

x"0000", x"0000", x"0000", x"0000",
x"0000", x"0000", x"0000", x"0000",
x"0000", x"0000", x"0000", x"0000",
x"0000", x"0000", x"0000", x"0000",

--module 1E
x"0000", x"0000", x"0000", x"0000",
x"0000", x"0000", x"0000", x"0000",
x"0000", x"0000", x"0000", x"0000",
x"0000", x"0000", x"0000", x"0000",

--module 1F
x"0000", x"0000", x"0000", x"0000",
x"0000", x"0000", x"0000", x"0000",
x"0000", x"0000", x"0000", x"0000",
x"0000", x"0000", x"0000", x"0000"
);

variable addr : integer range 0 to 511;
variable addr_out : STD_LOGIC_VECTOR(15 downto 0);

begin
    addr := conv_integer(address_mem(8 downto 0));
    addr_out := data_mem(addr);
    if mem_write = '1' then
        data_mem(addr) := write_data;
    else read_data <= addr_out;
    end if;
end process;

end Behavioral;

```

## 1.13 Microprogramme Controller

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MicroprogrammeController is
    Port( IR : in STD_LOGIC_VECTOR(15 downto 0);
          status_bits : in STD_LOGIC_VECTOR(3 downto 0);
          reset_mpc : in STD_LOGIC;
          control_word_mpc : out STD_LOGIC_VECTOR(17 downto 0);
          PC_out : out STD_LOGIC_VECTOR(15 downto 0);
          TD_mpc, TA_mpc, TB_mpc, MW_mpc : out STD_LOGIC
        );
end MicroprogrammeController;

architecture Behavioral of MicroprogrammeController is
    component ControlMemory
        Port( in_car : in STD_LOGIC_VECTOR(7 downto 0);
              MW, MM, RW, MD, MB, TB, TA, TD, PL, PI, IL, MC : out STD_LOGIC;
              FS_cm : out STD_LOGIC_VECTOR(4 downto 0);
              MS_cm : out STD_LOGIC_VECTOR(2 downto 0);
              NA : out STD_LOGIC_VECTOR(7 downto 0)
            );
    end component ControlMemory;

```



```

end component;

component Mux2to8
  Port( In0_NA, In1_opcode : in STD_LOGIC_VECTOR(7 downto 0);
        S_mc : in STD_LOGIC;
        out_car : out STD_LOGIC_VECTOR(7 downto 0)
        );
end component;

component Mux8to1
  Port( In_zero, In_one, In_n, In_z, In_c, In_v, In_not_c, In_not_z : in STD_LOGIC;
        S_ms : in STD_LOGIC_VECTOR(2 downto 0);
        out_s_car : out STD_LOGIC
        );
end component;

component ControlAddressRegister
  Port( car_in : in STD_LOGIC_VECTOR(7 downto 0);
        s_car, reset : in STD_LOGIC;
        car_out : out STD_LOGIC_VECTOR(7 downto 0)
        );
end component;

component Instructions
  Port( IR_in : in STD_LOGIC_VECTOR(15 downto 0);
        IL_in : in STD_LOGIC;
        Opcode : out STD_LOGIC_VECTOR(6 downto 0);
        DR_out, SA_out, SB_out : out STD_LOGIC_VECTOR(2 downto 0)
        );
end component;

component ProgrammeCounter
  Port( PC_module_in : in STD_LOGIC_VECTOR(15 downto 0);
        PL_module_in, PI_module_in, reset : in STD_LOGIC;
        PC_module_out : out STD_LOGIC_VECTOR(15 downto 0)
        );
end component;

component ExtendedProgrammeCounter
  Port( SR_SB : in STD_LOGIC_VECTOR(5 downto 0);
        ExtendedProgrammeCounter : out STD_LOGIC_VECTOR(15 downto 0)
        );
end component;

--signalling
signal control_word_sig : STD_LOGIC_VECTOR(17 downto 0);
signal opcode_sig, car_out_sig, out_car_sig, na_sig : STD_LOGIC_VECTOR(7 downto 0);
signal out_s_car_sig, mc_sig, il_sig, pl_sig, pi_sig : STD_LOGIC;
signal ms_cm_sig, sa_sig, sb_sig, dr_sig : STD_LOGIC_VECTOR(2 downto 0);
signal extend_in : STD_LOGIC_VECTOR(5 downto 0);
signal extend_out : STD_LOGIC_VECTOR(15 downto 0);

begin
  control_mem_mpc : ControlMemory PORT MAP(
    in_car => car_out_sig,

```

```

MW => mw_mpc,
MM => control_word_sig(0),
RW => control_word_sig(1),
MD => control_word_sig(2),
MB => control_word_sig(8),
TB => tb_mpc,
TA => ta_mpc,
TD => td_mpc,
PL => pl_sig,
PI => pi_sig,
IL => il_sig,
MC => mc_sig,
FS_cm => control_word_sig(7 downto 3),
MS_cm => ms_cm_sig,
NA => na_sig
);

mux2to8_mpc : mux2to8 PORT MAP(
    In0_NA => na_sig,
    In1_opcode => opcode_sig,
    S_mc => mc_sig,
    out_car => out_car_sig
);

mux8to1_mpc : Mux8to1 PORT MAP(
    In_zero => '0',
    In_one => '1',
    In_z => status_bits(0),
    In_n => status_bits(1),
    In_c => status_bits(2),
    In_v => status_bits(3),
    In_not_z => not status_bits(0),
    In_not_c => not status_bits(2),
    S_ms => ms_cm_sig,
    out_s_car => out_s_car_sig
);

car_mpc : ControlAddressRegister PORT MAP(
    car_in => out_car_sig,
    s_car => out_s_car_sig,
    reset => reset_mpc,
    car_out => car_out_sig
);

instructions_mpc : Instructions PORT MAP(
    IR_in => IR,
    IL_in => il_sig,
    Opcode => opcode_sig(6 downto 0),
    DR_out => dr_sig,
    SA_out => sa_sig,
    SB_out => sb_sig
);

extended_mpc : ExtendedProgrammeCounter PORT MAP(
    SR_SB => extend_in,

```

```

    ExtendedProgrammeCounter => extend_out
);

pc_mpc : ProgrammeCounter PORT MAP(
    PC_module_in => extend_out,
    PL_module_in => pl_sig,
    PI_module_in => pi_sig,
    reset => reset_mpc,
    PC_module_out => pc_out
);

extend_in(5 downto 3) <= dr_sig;
extend_in(2 downto 0) <= sb_sig;
opcode_sig(7) <= '0';

control_word_sig(17 downto 15) <= dr_sig;
control_word_sig(14 downto 12) <= sa_sig;
control_word_sig(11 downto 9) <= sb_sig;
control_word_mpc <= control_word_sig;

end Behavioral;

```

## 1.14 Mux 2-1 Bit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux2to1 is
    Port(
        B_i, S0, S1 : in STD_LOGIC;
        Y_i : out STD_LOGIC
    );
end Mux2to1;

architecture Behavioral of Mux2to1 is
begin
    Y_i <= S0 after 1ns when B_i = '1' else
           S1 after 1ns when B_i = '0' else
           '0' after 1ns;

end Behavioral;

```

## 1.15 Mux 2-8 Bit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux2to8 is
    Port( In0_NA, In1_opcode : in STD_LOGIC_VECTOR(7 downto 0);
          S_mc : in STD_LOGIC;
          out_car : out STD_LOGIC_VECTOR(7 downto 0)
    );
end Mux2to8;

```

```

architecture Behavioral of Mux2to8 is

begin
    out_car <= In0_NA after 1ns when S_mc='0' else
                In1_opcode after 1ns when S_mc='1' else
                x"00" after 20ns;

end Behavioral;

```

## 1.16 Mux 2-16 Bit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux2to16 is
    Port( In0, In1 : in STD_LOGIC_VECTOR(15 downto 0);
          s : in STD_LOGIC;
          Z : out STD_LOGIC_VECTOR(15 downto 0)
    );
end Mux2to16;

architecture Behavioral of Mux2to16 is

begin
    Z <= In0 after 1ns when s='0' else
          In1 after 1ns when s='1' else
          x"0000" after 1ns;

end Behavioral;

```

## 1.17 Mux 3-1 Bit

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux_3_1 is
    Port(
        In0, In1, In2 : in STD_LOGIC;
        S0, S1 : in STD_LOGIC;
        Z : out STD_LOGIC
    );
end mux_3_1;

architecture Behavioral of mux_3_1 is

begin
    Z <= In0 after 1ns when S0 = '0' and S1 = '0' else
          In1 after 1ns when S0 = '0' and S1 = '1' else
          In2 after 1ns when S0 = '1' and S1 = '0' else
          '0' after 1ns;

end Behavioral;

```

## 1.18 Mux 8-1 Bit

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux8to1 is
    Port( In_zero, In_one, In_n, In_z, In_c, In_v, In_not_c, In_not_z : in STD_LOGIC;
          S_ms : in STD_LOGIC_VECTOR(2 downto 0);
          out_s_car : out STD_LOGIC
        );
end Mux8to1;

architecture Behavioral of Mux8to1 is

begin
    out_s_car <= In_zero after 1ns when S_ms = "000" else
                 In_one after 1ns when S_ms = "001" else
                 In_c after 1ns when S_ms = "010" else
                 In_v after 1ns when S_ms = "011" else
                 In_z after 1ns when S_ms = "100" else
                 In_n after 1ns when S_ms = "101" else
                 In_not_c after 1ns when S_ms = "110" else
                 In_not_z after 1ns when S_ms = "111";

end Behavioral;
```

## 1.19 Mux 9-16 Bit

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux9to16 is
    Port( In0, In1, In2, In3, In4, In5, In6, In7, In8 : in STD_LOGIC_VECTOR(15 downto 0);
          S0, S1, S2, S3 : in STD_LOGIC;
          Z : out STD_LOGIC_VECTOR(15 downto 0)
        );
end Mux9to16;

architecture Behavioral of Mux9to16 is

begin
    Z <= In0 after 5ns when S0='0' and S1='0' and S2='0' and S3='0' else
         In1 after 5ns when S0='1' and S1='0' and S2='0' and S3='0' else
         In2 after 5ns when S0='0' and S1='1' and S2='0' and S3='0' else
         In3 after 5ns when S0='1' and S1='1' and S2='0' and S3='0' else
         In4 after 5ns when S0='0' and S1='0' and S2='1' and S3='0' else
         In5 after 5ns when S0='1' and S1='0' and S2='1' and S3='0' else
         In6 after 5ns when S0='0' and S1='1' and S2='1' and S3='0' else
         In7 after 5ns when S0='1' and S1='1' and S2='1' and S3='0' else
         In8 after 5ns when S0='0' and S1='0' and S2='0' and S3='1' else
         x"0000" after 5ns;

end Behavioral;
```

## 1.20 Programme Counter

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ProgrammeCounter is
    Port( PC_module_in : in STD_LOGIC_VECTOR(15 downto 0);
          PL_module_in, PI_module_in, reset : in STD_LOGIC;
          PC_module_out : out STD_LOGIC_VECTOR(15 downto 0)
        );
end ProgrammeCounter;

architecture Behavioral of ProgrammeCounter is
begin
    process(reset, PL_module_in, PI_module_in)
        variable current_PC : STD_LOGIC_VECTOR(15 downto 0);
        variable temp_curr_PC : integer;
        variable temp_inc_PC : STD_LOGIC_VECTOR(15 downto 0);

    begin
        if(reset = '1') then current_PC := x"0000";
        elsif(PL_module_in = '1') then
            current_PC := current_PC + PC_module_in;
        elsif(PI_module_in = '1') then
            temp_curr_PC := conv_integer(current_PC); -- get current allocation
            temp_curr_PC := temp_curr_PC + conv_integer(1); -- increment
            temp_inc_PC := conv_std_logic_vector(temp_curr_PC, 16); -- cast from int to vector
            current_PC := temp_inc_PC; -- store as current PC
        end if;
        PC_module_out <= current_PC after 2ns;
    end process;
end Behavioral;
```

## 1.21 Project 2 Top Level

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Proj2 is
    Port( Clk, reset : in STD_LOGIC
        );
end Proj2;

architecture Behavioral of Proj2 is

    component Datapath
        Port( data_in, pc_in : in STD_LOGIC_VECTOR(15 downto 0);
              control_word : in STD_LOGIC_VECTOR(17 downto 0);
              clk_sig, TD, TA, TB : in STD_LOGIC;
              data_out, addr_out : out STD_LOGIC_VECTOR(15 downto 0);
              status_out : out STD_LOGIC_VECTOR(3 downto 0)
            );
    end component;
```

```

end component;

component MicroprogrammeController
  Port( IR : in STD_LOGIC_VECTOR(15 downto 0);
        status_bits : in STD_LOGIC_VECTOR(3 downto 0);
        reset_mpc : in STD_LOGIC;
        control_word_mpc : out STD_LOGIC_VECTOR(17 downto 0);
        PC_out : out STD_LOGIC_VECTOR(15 downto 0);
        TD_mpc, TA_mpc, TB_mpc, MW_mpc : out STD_LOGIC
        );
end component;

component Memory
  Port( address_mem : in STD_LOGIC_VECTOR(15 downto 0);
        write_data : in STD_LOGIC_VECTOR(15 downto 0);
        mem_write : in STD_LOGIC;
        read_data : out STD_LOGIC_VECTOR(15 downto 0)
        );
end component;

signal mm_read_data, mpc_pc_out, dp_data_out, dp_address_out : STD_LOGIC_VECTOR(15 downto
  0);
signal mpc_control_word : STD_LOGIC_VECTOR(17 downto 0);
signal dp_status_out : STD_LOGIC_VECTOR(3 downto 0);
signal mpc_TD, mpc_TA, mpc_TB, mpc_MW : STD_LOGIC;

begin
  data_path : Datapath PORT MAP(
    data_in => mm_read_data,
    pc_in => mpc_pc_out,
    control_word => mpc_control_word,
    clk_sig => Clk,
    TD => mpc_TD,
    TA => mpc_TA,
    TB => mpc_TB,
    data_out => dp_data_out,
    addr_out => dp_address_out,
    status_out => dp_status_out
  );

  micro_pc : MicroprogrammeController PORT MAP(
    IR => mm_read_data,
    status_bits => dp_status_out,
    reset_mpc => reset,
    control_word_mpc => mpc_control_word,
    PC_out => mpc_pc_out,
    TD_mpc => mpc_TD,
    TA_mpc => mpc_TA,
    TB_mpc => mpc_TB,
    MW_mpc => mpc_MW
  );

  memory_module : Memory PORT MAP(
    address_mem => dp_address_out,
    write_data => dp_data_out,

```

```

        mem_write => mpc_MW,
        read_data => mm_read_data
    );

end Behavioral;

```

## 1.22 Register

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Reg16 is
    Port( D : in STD_LOGIC_VECTOR(15 downto 0);
          load0, load1, Clk : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR(15 downto 0)
    );
end Reg16;

architecture Behavioral of Reg16 is

begin
    process (Clk)
    begin
        if(rising_edge(Clk)) then
            if((load0 = '1') and (load1 = '1')) then
                Q <= D after 5ns;
            end if;
        end if;
    end process;

end Behavioral;

```

## 1.23 Register File

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RegFile is
    Port( des_d, add_a, add_b : in STD_LOGIC_VECTOR(3 downto 0);
          Clk, load_in : in STD_LOGIC;
          data : in STD_LOGIC_VECTOR(15 downto 0);
          out_data_a, out_data_b : out STD_LOGIC_VECTOR(15 downto 0)
    );
end RegFile;

architecture Behavioral of RegFile is
    component Reg16
        Port( D : in STD_LOGIC_VECTOR(15 downto 0);
              load0, load1, Clk : in STD_LOGIC;
              Q : out STD_LOGIC_VECTOR(15 downto 0)
        );
    end component;

    component Decoder4to9
        Port( A0, A1, A2, A3 : in STD_LOGIC;

```



```

        Q0, Q1, Q2, Q3, Q4, Q5, Q6, Q7, Q8 : out STD_LOGIC
    );
end component;

component Mux2to16
    Port( In0, In1 : in STD_LOGIC_VECTOR(15 downto 0);
          s : in STD_LOGIC;
          Z : out STD_LOGIC_VECTOR(15 downto 0)
    );
end component;

component Mux9to16
    Port( In0, In1, In2, In3, In4, In5, In6, In7, In8 : in STD_LOGIC_VECTOR(15 downto 0);
          S0, S1, S2 : in STD_LOGIC;
          Z : out STD_LOGIC_VECTOR(15 downto 0)
    );
end component;

signal load_reg0, load_reg1, load_reg2, load_reg3, load_reg4, load_reg5, load_reg6,
        load_reg7, load_reg8 : STD_LOGIC;
signal reg0_q, reg1_q, reg2_q, reg3_q, reg4_q, reg5_q, reg6_q, reg7_q, reg8_q, out_sig_a,
        out_sig_b : STD_LOGIC_VECTOR(15 downto 0);

begin
    --reg0
    reg0: Reg16 PORT MAP(
        D => data,
        load0 => load_reg0,
        load1 => load_in,
        Clk => Clk,
        Q => reg0_q
    );

    --reg1
    reg1: Reg16 PORT MAP(
        D => data,
        load0 => load_reg1,
        load1 => load_in,
        Clk => Clk,
        Q => reg1_q
    );

    --reg2
    reg2: Reg16 PORT MAP(
        D => data,
        load0 => load_reg2,
        load1 => load_in,
        Clk => Clk,
        Q => reg2_q
    );

    --reg3
    reg3: Reg16 PORT MAP(
        D => data,
        load0 => load_reg3,

```

```

    load1 => load_in,
    Clk => Clk,
    Q => reg3_q
);

--reg4
reg4: Reg16 PORT MAP(
    D => data,
    load0 => load_reg4,
    load1 => load_in,
    Clk => Clk,
    Q => reg4_q
);

--reg5
reg5: Reg16 PORT MAP(
    D => data,
    load0 => load_reg5,
    load1 => load_in,
    Clk => Clk,
    Q => reg5_q
);

--reg6
reg6: Reg16 PORT MAP(
    D => data,
    load0 => load_reg6,
    load1 => load_in,
    Clk => Clk,
    Q => reg6_q
);

--reg7
reg7: Reg16 PORT MAP(
    D => data,
    load0 => load_reg7,
    load1 => load_in,
    Clk => Clk,
    Q => reg7_q
);

--reg8
reg8: Reg16 PORT MAP(
    D => data,
    load0 => load_reg8,
    load1 => load_in,
    Clk => Clk,
    Q => reg8_q
);

DesDecoder4to9 : Decoder4to9 PORT MAP(
    A0 => des_d(0),
    A1 => des_d(1),
    A2 => des_d(2),
    A3 => des_d(3),

```

```

    Q0 => load_reg0,
    Q1 => load_reg1,
    Q2 => load_reg2,
    Q3 => load_reg3,
    Q4 => load_reg4,
    Q5 => load_reg5,
    Q6 => load_reg6,
    Q7 => load_reg7,
    Q8 => load_reg8
);

Mux9to16A : Mux9to16 PORT MAP(
    In0 => reg0_q,
    In1 => reg1_q,
    In2 => reg2_q,
    In3 => reg3_q,
    In4 => reg4_q,
    In5 => reg5_q,
    In6 => reg6_q,
    In7 => reg7_q,
    In8 => reg8_q,
    S0 => add_b(0),
    S1 => add_b(1),
    S2 => add_b(2),
    Z => out_sig_a
);

Mux9to16B : Mux9to16 PORT MAP(
    In0 => reg0_q,
    In1 => reg1_q,
    In2 => reg2_q,
    In3 => reg3_q,
    In4 => reg4_q,
    In5 => reg5_q,
    In6 => reg6_q,
    In7 => reg7_q,
    In8 => reg8_q,
    S0 => add_b(0),
    S1 => add_b(1),
    S2 => add_b(2),
    Z => out_sig_b
);

out_data_a <= out_sig_a;
out_data_b <= out_sig_b;

end Behavioral;

```

## 1.24 Ripple Adder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RippleAdder is
    Port(
        A, B : in STD_LOGIC_VECTOR(15 downto 0);
        Cin : STD_LOGIC;
        Cout, V_out : out STD_LOGIC;
        G_out : out STD_LOGIC_VECTOR(15 downto 0)
    );

end RippleAdder;

architecture Behavioral of RippleAdder is

    Component FullAdder
        Port(
            X, Y, Cin : in STD_LOGIC;
            Cout, S : out STD_LOGIC
        );
    End Component;

    --signals - 16 carry bits and 1 output
    signal C0, C1, C2, C3, C4, C5, C6, C7, C8, C9, C10, C11, C12, C13, C14, C15, C_out :
        STD_LOGIC;

begin
    full_adder_00: FullAdder PORT MAP(
        X => A(0),
        Y => B(0),
        Cin => Cin,
        Cout => C0,
        S => G_out(0)
    );

    full_adder_01: FullAdder PORT MAP(
        X => A(1),
        Y => B(1),
        Cin => C0,
        Cout => C1,
        S => G_out(1)
    );

    full_adder_02: FullAdder PORT MAP(
        X => A(2),
        Y => B(2),
        Cin => C1,
        Cout => C2,
        S => G_out(2)
    );

    full_adder_03: FullAdder PORT MAP(
        X => A(3),
```

```

    Y => B(3),
    Cin => C2,
    Cout => C3,
    S => G_out(3)
);

full_adder_04: FullAdder PORT MAP(
    X => A(4),
    Y => B(4),
    Cin => C3,
    Cout => C4,
    S => G_out(4)
);

full_adder_05: FullAdder PORT MAP(
    X => A(5),
    Y => B(5),
    Cin => C4,
    Cout => C5,
    S => G_out(5)
);

full_adder_06: FullAdder PORT MAP(
    X => A(6),
    Y => B(6),
    Cin => C5,
    Cout => C6,
    S => G_out(6)
);

full_adder_07: FullAdder PORT MAP(
    X => A(7),
    Y => B(7),
    Cin => C6,
    Cout => C7,
    S => G_out(7)
);

full_adder_08: FullAdder PORT MAP(
    X => A(8),
    Y => B(8),
    Cin => C7,
    Cout => C8,
    S => G_out(8)
);

full_adder_09: FullAdder PORT MAP(
    X => A(9),
    Y => B(9),
    Cin => C8,
    Cout => C9,
    S => G_out(9)
);

full_adder_10: FullAdder PORT MAP(

```

```

    X => A(10),
    Y => B(10),
    Cin => C9,
    Cout => C10,
    S => G_out(10)
);

full_adder_11: FullAdder PORT MAP(
    X => A(11),
    Y => B(11),
    Cin => C10,
    Cout => C11,
    S => G_out(11)
);

full_adder_12: FullAdder PORT MAP(
    X => A(12),
    Y => B(12),
    Cin => C11,
    Cout => C12,
    S => G_out(12)
);

full_adder_13: FullAdder PORT MAP(
    X => A(13),
    Y => B(13),
    Cin => C12,
    Cout => C13,
    S => G_out(13)
);

full_adder_14: FullAdder PORT MAP(
    X => A(14),
    Y => B(14),
    Cin => C13,
    Cout => C14,
    S => G_out(14)
);

full_adder_15: FullAdder PORT MAP(
    X => A(15),
    Y => B(15),
    Cin => C14,
    Cout => C15,
    S => G_out(15)
);

--carry
Cout <= C_out;
--overflow
V_out <= (C_out xor C15);

end Behavioral;

```

## 1.25 Shifter

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity shifter is
  Port(
    B : in STD_LOGIC_VECTOR(15 downto 0);
    S : in STD_LOGIC_VECTOR(1 downto 0);
    IL, IR : in STD_LOGIC;
    H : out STD_LOGIC_VECTOR(15 downto 0)
  );
end shifter;

architecture Behavioral of shifter is

  --2 to 1 mux
  Component mux_3_1
    Port(
      In0, In1, In2, S0, S1 : in STD_LOGIC;
      Z : out STD_LOGIC
    );
  End Component;

begin
  mux00: mux_3_1 PORT MAP(
    In0 => B(0),
    In1 => B(1),
    In2 => IL,
    S0 => S(0),
    S1 => S(1),
    Z => H(0)
  );

  mux01: mux_3_1 PORT MAP(
    In0 => B(1),
    In1 => B(2),
    In2 => B(0),
    S0 => S(0),
    S1 => S(1),
    Z => H(1)
  );

  mux02: mux_3_1 PORT MAP(
    In0 => B(2),
    In1 => B(3),
    In2 => B(1),
    S0 => S(0),
    S1 => S(1),
    Z => H(2)
  );

  mux03: mux_3_1 PORT MAP(
    In0 => B(3),
    In1 => B(4),
```

```

    In2 => B(2),
    S0 => S(0),
    S1 => S(1),
    Z => H(3)
);

mux04: mux_3_1 PORT MAP(
    In0 => B(4),
    In1 => B(5),
    In2 => B(3),
    S0 => S(0),
    S1 => S(1),
    Z => H(4)
);

mux05: mux_3_1 PORT MAP(
    In0 => B(5),
    In1 => B(6),
    In2 => B(4),
    S0 => S(0),
    S1 => S(1),
    Z => H(5)
);

mux06: mux_3_1 PORT MAP(
    In0 => B(6),
    In1 => B(7),
    In2 => B(5),
    S0 => S(0),
    S1 => S(1),
    Z => H(6)
);

mux07: mux_3_1 PORT MAP(
    In0 => B(7),
    In1 => B(8),
    In2 => B(6),
    S0 => S(0),
    S1 => S(1),
    Z => H(7)
);

mux08: mux_3_1 PORT MAP(
    In0 => B(8),
    In1 => B(9),
    In2 => B(7),
    S0 => S(0),
    S1 => S(1),
    Z => H(8)
);

mux09: mux_3_1 PORT MAP(
    In0 => B(9),
    In1 => B(10),
    In2 => B(8),

```



```

    S0 => S(0),
    S1 => S(1),
    Z => H(9)
);

mux10: mux_3_1 PORT MAP(
    In0 => B(10),
    In1 => B(11),
    In2 => B(9),
    S0 => S(0),
    S1 => S(1),
    Z => H(10)
);

mux11: mux_3_1 PORT MAP(
    In0 => B(11),
    In1 => B(12),
    In2 => B(10),
    S0 => S(0),
    S1 => S(1),
    Z => H(11)
);

mux12: mux_3_1 PORT MAP(
    In0 => B(12),
    In1 => B(13),
    In2 => B(11),
    S0 => S(0),
    S1 => S(1),
    Z => H(12)
);

mux13: mux_3_1 PORT MAP(
    In0 => B(13),
    In1 => B(14),
    In2 => B(12),
    S0 => S(0),
    S1 => S(1),
    Z => H(13)
);

mux14: mux_3_1 PORT MAP(
    In0 => B(14),
    In1 => B(15),
    In2 => B(13),
    S0 => S(0),
    S1 => S(1),
    Z => H(14)
);

mux15: mux_3_1 PORT MAP(
    In0 => B(15),
    In1 => IR,
    In2 => B(14),
    S0 => S(0),

```

```

        S1 => S(1),
        Z => H(15)
    );

```

```

end Behavioral;

```

## 1.26 Zero Fill

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ZeroFill is
    Port( SB_in : in STD_LOGIC_VECTOR(2 downto 0);
          zero_fill_out : out STD_LOGIC_VECTOR(15 downto 0)
        );
end ZeroFill;

architecture Behavioral of ZeroFill is
    signal ZeroFill : STD_LOGIC_VECTOR(15 downto 0);
begin
    ZeroFill(2 downto 0) <= SB_in;
    ZeroFill(15 downto 3) <= "0000000000000";
end Behavioral;

```

## 2 Component Test Benches

### 2.1 Control Address Register

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY ControlAddressRegister_TB IS
END ControlAddressRegister_TB;

ARCHITECTURE behavior OF ControlAddressRegister_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT ControlAddressRegister
    PORT(
        car_in : IN std_logic_vector(7 downto 0);
        s_car : IN std_logic;
        reset : IN std_logic;
        car_out : OUT std_logic_vector(7 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal car_in : std_logic_vector(7 downto 0) := (others => '0');
    signal s_car : std_logic := '0';
    signal reset : std_logic := '0';

    --Outputs
    signal car_out : std_logic_vector(7 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: ControlAddressRegister PORT MAP (
        car_in => car_in,
        s_car => s_car,
        reset => reset,
        car_out => car_out
    );

    -- Stimulus process
    stim_proc: process
    begin
        wait for 5ns;
        reset <= '1';

        wait for 30ns;
        reset <= '0';

        wait for 30ns;
        car_in <= x"01";

        wait for 30ns;
```

```

    car_in <= x"A1";
    s_car <= '1';

    wait;
end process;

END;

```

## 2.2 Control Memory

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY ControlMemory_TB IS
END ControlMemory_TB;

ARCHITECTURE behavior OF ControlMemory_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT ControlMemory
    PORT(
        in_car : IN std_logic_vector(7 downto 0);
        MW : OUT std_logic;
        MM : OUT std_logic;
        RW : OUT std_logic;
        MD : OUT std_logic;
        MB : OUT std_logic;
        TB : OUT std_logic;
        TA : OUT std_logic;
        TD : OUT std_logic;
        PL : OUT std_logic;
        PI : OUT std_logic;
        IL : OUT std_logic;
        MC : OUT std_logic;
        FS_cm : OUT std_logic_vector(4 downto 0);
        MS_cm : OUT std_logic_vector(2 downto 0);
        NA : OUT std_logic_vector(7 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal in_car : std_logic_vector(7 downto 0) := (others => '0');

    --Outputs
    signal MW : std_logic;
    signal MM : std_logic;
    signal RW : std_logic;
    signal MD : std_logic;
    signal MB : std_logic;
    signal TB : std_logic;
    signal TA : std_logic;
    signal TD : std_logic;
    signal PL : std_logic;

```

```

signal PI : std_logic;
signal IL : std_logic;
signal MC : std_logic;
signal FS_cm : std_logic_vector(4 downto 0);
signal MS_cm : std_logic_vector(2 downto 0);
signal NA : std_logic_vector(7 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: ControlMemory PORT MAP (
        in_car => in_car,
        MW => MW,
        MM => MM,
        RW => RW,
        MD => MD,
        MB => MB,
        TB => TB,
        TA => TA,
        TD => TD,
        PL => PL,
        PI => PI,
        IL => IL,
        MC => MC,
        FS_cm => FS_cm,
        MS_cm => MS_cm,
        NA => NA
    );

    -- Stimulus process
    stim_proc: process
    begin
        wait for 10ns;
        in_car <= x"00";

        wait for 10ns;
        in_car <= x"08";

        wait for 10ns;
        in_car <= x"0D";

        wait;
    end process;

END;
```

## 2.3 Decoder 4-9 bit

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Decoder4to9_TB IS
END Decoder4to9_TB;

ARCHITECTURE behavior OF Decoder4to9_TB IS
```

```

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT Decoder4to9
PORT(
    A0 : IN std_logic;
    A1 : IN std_logic;
    A2 : IN std_logic;
    A3 : IN std_logic;
    Q0 : OUT std_logic;
    Q1 : OUT std_logic;
    Q2 : OUT std_logic;
    Q3 : OUT std_logic;
    Q4 : OUT std_logic;
    Q5 : OUT std_logic;
    Q6 : OUT std_logic;
    Q7 : OUT std_logic;
    Q8 : OUT std_logic
);
END COMPONENT;

--Inputs
signal A0 : std_logic := '0';
signal A1 : std_logic := '0';
signal A2 : std_logic := '0';
signal A3 : std_logic := '0';

--Outputs
signal Q0 : std_logic;
signal Q1 : std_logic;
signal Q2 : std_logic;
signal Q3 : std_logic;
signal Q4 : std_logic;
signal Q5 : std_logic;
signal Q6 : std_logic;
signal Q7 : std_logic;
signal Q8 : std_logic;

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: Decoder4to9 PORT MAP (
    A0 => A0,
    A1 => A1,
    A2 => A2,
    A3 => A3,
    Q0 => Q0,
    Q1 => Q1,
    Q2 => Q2,
    Q3 => Q3,
    Q4 => Q4,
    Q5 => Q5,
    Q6 => Q6,
    Q7 => Q7,

```

```

        Q8 => Q8
    );

-- Stimulus process
stim_proc: process
begin
    wait for 5ns;
    A0 <= '0';
    A1 <= '0';
    A2 <= '0';
    A3 <= '0';

    wait for 5ns;
    A0 <= '1';
    A1 <= '0';
    A2 <= '0';
    A3 <= '0';

    wait for 5ns;
    A0 <= '0';
    A1 <= '1';
    A2 <= '0';
    A3 <= '0';

    wait for 5ns;
    A0 <= '1';
    A1 <= '1';
    A2 <= '0';
    A3 <= '0';

    wait for 5ns;
    A0 <= '0';
    A1 <= '0';
    A2 <= '1';
    A3 <= '0';

    wait for 5ns;
    A0 <= '1';
    A1 <= '0';
    A2 <= '1';
    A3 <= '0';

    wait for 5ns;
    A0 <= '0';
    A1 <= '1';
    A2 <= '1';
    A3 <= '0';

    wait for 5ns;
    A0 <= '1';
    A1 <= '1';
    A2 <= '1';
    A3 <= '0';

    wait for 5ns;

```

```

A3 <= '1';

wait for 5ns;
A0 <= '0';
A1 <= '0';
A2 <= '0';

wait for 5ns;
A0 <= '1';
A1 <= '0';
A2 <= '0';

wait for 5ns;
A0 <= '0';
A1 <= '1';
A2 <= '0';
end process;

END;

```

## 2.4 Extended Programme Counter

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY ExtendedProgrammeCounter_TB IS
END ExtendedProgrammeCounter_TB;

ARCHITECTURE behavior OF ExtendedProgrammeCounter_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT ExtendedProgrammeCounter
    PORT(
        SR_SB : IN std_logic_vector(5 downto 0);
        ExtendedProgrammeCounter : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal SR_SB : std_logic_vector(5 downto 0) := (others => '0');

    --Outputs
    signal ExtendedProgrammeCounter : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: ExtendedProgrammeCounter PORT MAP (
        SR_SB => SR_SB,
        ExtendedProgrammeCounter => ExtendedProgrammeCounter
    );

    -- Stimulus process

```



```

stim_proc: process
begin
    wait for 10ns;
    SR_SB <= "010110";

    wait for 10ns;
    SR_SB <= "110110";

    wait;
end process;

END;

```

## 2.5 Instruction Register

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Instructions_TB IS
END Instructions_TB;

ARCHITECTURE behavior OF Instructions_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Instructions
    PORT(
        IR_in : IN std_logic_vector(15 downto 0);
        IL_in : IN std_logic;
        Opcode : OUT std_logic_vector(6 downto 0);
        DR_out : OUT std_logic_vector(2 downto 0);
        SA_out : OUT std_logic_vector(2 downto 0);
        SB_out : OUT std_logic_vector(2 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal IR_in : std_logic_vector(15 downto 0) := (others => '0');
    signal IL_in : std_logic := '0';

    --Outputs
    signal Opcode : std_logic_vector(6 downto 0);
    signal DR_out : std_logic_vector(2 downto 0);
    signal SA_out : std_logic_vector(2 downto 0);
    signal SB_out : std_logic_vector(2 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Instructions PORT MAP (
        IR_in => IR_in,
        IL_in => IL_in,
        Opcode => Opcode,
        DR_out => DR_out,

```

```

        SA_out => SA_out,
        SB_out => SB_out
    );

-- Stimulus process
stim_proc: process
begin
    wait for 10ns;
    IR_in <= "1111111000001010";

    wait for 5ns;
    IL_in <= '1';

    wait for 10ns;
    IR_in <= "0000000110110000";
    IL_in <= '0';

    wait for 5ns;
    IL_in <= '1';

    wait;
end process;

END;

```

## 2.6 Memory Module

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Memory_TB IS
END Memory_TB;

ARCHITECTURE behavior OF Memory_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Memory
    PORT(
        address_mem : IN std_logic_vector(15 downto 0);
        write_data : IN std_logic_vector(15 downto 0);
        mem_write : IN std_logic;
        read_data : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal address_mem : std_logic_vector(15 downto 0) := (others => '0');
    signal write_data : std_logic_vector(15 downto 0) := (others => '0');
    signal mem_write : std_logic := '0';

    --Outputs
    signal read_data : std_logic_vector(15 downto 0);

```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: Memory PORT MAP (  
    address_mem => address_mem,  
    write_data => write_data,  
    mem_write => mem_write,  
    read_data => read_data  
);
```

```
-- Stimulus process
```

```
stim_proc: process  
begin  
    wait for 10ns;  
    address_mem <= x"0000";  
  
    wait for 10ns;  
    address_mem <= x"0001";  
  
    wait for 10ns;  
    address_mem <= x"0006";  
  
    wait for 10ns;  
    address_mem <= x"0007";  
  
    wait;  
end process;
```

```
END;
```

## 2.7 Mux 2-8 Bit

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;
```

```
ENTITY Mux2to8_TB IS  
END Mux2to8_TB;
```

```
ARCHITECTURE behavior OF Mux2to8_TB IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT Mux2to8  
PORT(  
    In0_NA : IN std_logic_vector(7 downto 0);  
    In1_opcode : IN std_logic_vector(7 downto 0);  
    S_mc : IN std_logic;  
    out_car : OUT std_logic_vector(7 downto 0)  
);  
END COMPONENT;
```

```
--Inputs
```

```
signal In0_NA : std_logic_vector(7 downto 0) := (others => '0');  
signal In1_opcode : std_logic_vector(7 downto 0) := (others => '0');
```

```

signal S_mc : std_logic := '0';

--Outputs
signal out_car : std_logic_vector(7 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Mux2to8 PORT MAP (
        In0_NA => In0_NA,
        In1_opcode => In1_opcode,
        S_mc => S_mc,
        out_car => out_car
    );

    -- Stimulus process
    stim_proc: process
    begin
        In0_NA <= x"FF";
        In1_opcode <= x"AA";

        wait for 20ns;
        S_mc <= '1';

        wait;
    end process;

END;

```

## 2.8 Mux 8-1 Bit

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Mux8to1_TB IS
END Mux8to1_TB;

ARCHITECTURE behavior OF Mux8to1_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Mux8to1
    PORT(
        In_zero : IN std_logic;
        In_one : IN std_logic;
        In_n : IN std_logic;
        In_z : IN std_logic;
        In_c : IN std_logic;
        In_v : IN std_logic;
        In_not_c : IN std_logic;
        In_not_z : IN std_logic;
        S_ms : IN std_logic_vector(2 downto 0);
        out_s_car : OUT std_logic
    );
END COMPONENT;

```

```

--Inputs
signal In_zero : std_logic := '0';
signal In_one : std_logic := '0';
signal In_n : std_logic := '0';
signal In_z : std_logic := '0';
signal In_c : std_logic := '0';
signal In_v : std_logic := '0';
signal In_not_c : std_logic := '0';
signal In_not_z : std_logic := '0';
signal S_ms : std_logic_vector(2 downto 0) := (others => '0');

--Outputs
signal out_s_car : std_logic;

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: Mux8to1 PORT MAP (
    In_zero => In_zero,
    In_one => In_one,
    In_n => In_n,
    In_z => In_z,
    In_c => In_c,
    In_v => In_v,
    In_not_c => In_not_c,
    In_not_z => In_not_z,
    S_ms => S_ms,
    out_s_car => out_s_car
 );

-- Stimulus process
stim_proc: process
begin
    wait for 5ns;
    In_one <= '1';
    In_c <= '1';
    In_v <= '1';
    In_not_z <= '1';

    wait for 5ns;
    S_ms <= "001";

    wait for 5ns;
    S_ms <= "010";

    wait for 5ns;
    S_ms <= "011";

    wait for 5ns;
    S_ms <= "100";

    wait for 5ns;
    S_ms <= "101";

```

```

    wait for 5ns;
    S_ms <= "110";

    wait for 5ns;
    S_ms <= "111";

    wait for 5ns;

    wait;
end process;

END;

```

## 2.9 Mux 9-16 Bit

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

ENTITY Mux9to16_TB IS
END Mux9to16_TB;

```

```

ARCHITECTURE behavior OF Mux9to16_TB IS

```

```

    -- Component Declaration for the Unit Under Test (UUT)

```

```

COMPONENT Mux9to16
PORT(
    In0 : IN std_logic_vector(15 downto 0);
    In1 : IN std_logic_vector(15 downto 0);
    In2 : IN std_logic_vector(15 downto 0);
    In3 : IN std_logic_vector(15 downto 0);
    In4 : IN std_logic_vector(15 downto 0);
    In5 : IN std_logic_vector(15 downto 0);
    In6 : IN std_logic_vector(15 downto 0);
    In7 : IN std_logic_vector(15 downto 0);
    In8 : IN std_logic_vector(15 downto 0);
    S0 : IN std_logic;
    S1 : IN std_logic;
    S2 : IN std_logic;
    S3 : IN std_logic;
    Z : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

```

```

--Inputs

```

```

signal In0 : std_logic_vector(15 downto 0) := (others => '0');
signal In1 : std_logic_vector(15 downto 0) := (others => '0');
signal In2 : std_logic_vector(15 downto 0) := (others => '0');
signal In3 : std_logic_vector(15 downto 0) := (others => '0');
signal In4 : std_logic_vector(15 downto 0) := (others => '0');
signal In5 : std_logic_vector(15 downto 0) := (others => '0');
signal In6 : std_logic_vector(15 downto 0) := (others => '0');
signal In7 : std_logic_vector(15 downto 0) := (others => '0');

```

```

signal In8 : std_logic_vector(15 downto 0) := (others => '0');
signal S0 : std_logic := '0';
signal S1 : std_logic := '0';
signal S2 : std_logic := '0';
signal S3 : std_logic := '0';

--Outputs
signal Z : std_logic_vector(15 downto 0);

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: Mux9to16 PORT MAP (
    In0 => In0,
    In1 => In1,
    In2 => In2,
    In3 => In3,
    In4 => In4,
    In5 => In5,
    In6 => In6,
    In7 => In7,
    In8 => In8,
    S0 => S0,
    S1 => S1,
    S2 => S2,
    S3 => S3,
    Z => Z
  );

-- Stimulus process
stim_proc: process
begin
  In0 <= x"FFFF";
  In1 <= x"EEEE";
  In2 <= x"DDDD";
  In3 <= x"CCCC";
  In4 <= x"BBBB";
  In5 <= x"AAAA";
  In6 <= x"9999";
  In7 <= x"8888";
  In8 <= x"7777";

  wait for 10ns;
  S0 <= '1';
  S1 <= '0';
  S2 <= '0';

  wait for 10ns;
  S0 <= '0';
  S1 <= '1';
  S2 <= '0';

  wait for 10ns;
  S0 <= '1';
  S1 <= '1';

```

```

S2 <= '0';

wait for 10ns;
S0 <= '0';
S1 <= '0';
S2 <= '1';

wait for 10ns;
S0 <= '1';
S1 <= '0';
S2 <= '1';

wait for 10ns;
S0 <= '0';
S1 <= '1';
S2 <= '1';

wait for 10ns;
S0 <= '1';
S1 <= '1';
S2 <= '1';

wait for 10ns;
S3 <= '1';

wait for 10ns;
S0 <= '1';
S1 <= '0';
S2 <= '0';

wait for 10ns;
S0 <= '0';
S1 <= '1';
S2 <= '0';

wait for 10ns;
S0 <= '1';
S1 <= '1';
S2 <= '0';

end process;

END;

```

## 2.10 Programme Counter

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY ProgrammeCounter_TB IS
END ProgrammeCounter_TB;

ARCHITECTURE behavior OF ProgrammeCounter_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

```



```

COMPONENT ProgrammeCounter
PORT(
    PC_module_in : IN std_logic_vector(15 downto 0);
    PL_module_in : IN std_logic;
    PI_module_in : IN std_logic;
    reset : IN std_logic;
    PC_module_out : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

--Inputs
signal PC_module_in : std_logic_vector(15 downto 0) := (others => '0');
signal PL_module_in : std_logic := '0';
signal PI_module_in : std_logic := '0';
signal reset : std_logic := '0';

--Outputs
signal PC_module_out : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: ProgrammeCounter PORT MAP (
        PC_module_in => PC_module_in,
        PL_module_in => PL_module_in,
        PI_module_in => PI_module_in,
        reset => reset,
        PC_module_out => PC_module_out
    );

    -- Stimulus process
    stim_proc: process
    begin
        wait for 5ns;
        reset <= '1';
        PC_module_in <= x"0000";

        wait for 5ns;
        reset <= '0';

        wait for 5ns;
        PI_module_in <= '1';
        PC_module_in <= x"0002";

        wait for 20ns;
        PI_module_in <= '0';
        PL_module_in <= '1';
        PC_module_in <= x"000F";

        wait;
    end process;

END;

```

## 2.11 Project 2 Top Level

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY Proj2_TB IS
END Proj2_TB;

ARCHITECTURE behavior OF Proj2_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Proj2
    PORT(
        Clk : IN std_logic;
        reset : IN std_logic
    );
    END COMPONENT;

    --Inputs
    signal Clk : std_logic := '0';
    signal reset : std_logic := '0';

    -- Clock period definitions
    constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Proj2 PORT MAP (
        Clk => Clk,
        reset => reset
    );

    -- Clock process definitions
    Clk_process :process
    begin
        Clk <= '0';
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        reset <= '1';
        wait for 40ns;

        reset <= '0';
        wait;
    end process;
END;
```

## 2.12 Register File

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY RegFile_TB IS
END RegFile_TB;

ARCHITECTURE behavior OF RegFile_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT RegFile
    PORT(
        des_d : IN std_logic_vector(3 downto 0);
        add_a : IN std_logic_vector(3 downto 0);
        add_b : IN std_logic_vector(3 downto 0);
        Clk : IN std_logic;
        load_in : IN std_logic;
        data : IN std_logic_vector(15 downto 0);
        out_data_a : OUT std_logic_vector(15 downto 0);
        out_data_b : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal des_d : std_logic_vector(3 downto 0) := (others => '0');
    signal add_a : std_logic_vector(3 downto 0) := (others => '0');
    signal add_b : std_logic_vector(3 downto 0) := (others => '0');
    signal Clk : std_logic := '0';
    signal load_in : std_logic := '0';
    signal data : std_logic_vector(15 downto 0) := (others => '0');

    --Outputs
    signal out_data_a : std_logic_vector(15 downto 0);
    signal out_data_b : std_logic_vector(15 downto 0);

    -- Clock period definitions
    constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: RegFile PORT MAP (
        des_d => des_d,
        add_a => add_a,
        add_b => add_b,
        Clk => Clk,
        load_in => load_in,
        data => data,
        out_data_a => out_data_a,
        out_data_b => out_data_b
    );
```

```
-- Clock process definitions
```

```
Clk_process :process
```

```
begin
```

```
    Clk <= '0';
```

```
    wait for Clk_period/2;
```

```
    Clk <= '1';
```

```
    wait for Clk_period/2;
```

```
end process;
```

```
-- Stimulus process
```

```
stim_proc: process
```

```
begin
```

```
    load_in <= '1'
```

```
    des_d <= "0000";
```

```
    data <= x"FFFF";
```

```
    wait for 10ns;
```

```
    des_d <= "0001";
```

```
    data <= x"EEEE";
```

```
    wait for 10ns;
```

```
    des_d <= "0010";
```

```
    data <= x"DDDD";
```

```
    wait for 10ns;
```

```
    des_d <= "0011";
```

```
    data <= x"CCCC";
```

```
    wait for 10ns;
```

```
    des_d <= "0100";
```

```
    data <= x"BBBB";
```

```
    wait for 10ns;
```

```
    des_d <= "0101";
```

```
    data <= x"AAAA";
```

```
    wait for 10ns;
```

```
    des_d <= "0110";
```

```
    data <= x"9999";
```

```
    wait for 10ns;
```

```
    des_d <= "0111";
```

```
    data <= x"8888";
```

```
    wait for 10ns;
```

```
    des_d <= "1000";
```

```
    data <= x"7777";
```

```
    wait for 10ns;
```

```
    load_in <= '0';
```

```
    add_a <= "0000";
```

```
    add_b <= "0111";
```

```
    wait for 5ns;
```

```
    add_a <= "0001";
```

```

    add_b <= "0110";
    wait for 5ns;

    add_a <= "0010";
    add_b <= "0101";
    wait for 5ns;

    add_a <= "0011";
    add_b <= "0100";
    wait for 5ns;

    add_a <= "1000";
    add_b <= "1111";
    wait for 5ns;

    wait;
end process;
END;

```

## 2.13 Zero Fill

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY ZeroFill_TB IS
END ZeroFill_TB;

ARCHITECTURE behavior OF ZeroFill_TB IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT ZeroFill
    PORT(
        SB_in : IN std_logic_vector(2 downto 0);
        zero_fill_out : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal SB_in : std_logic_vector(2 downto 0) := (others => '0');

    --Outputs
    signal zero_fill_out : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: ZeroFill PORT MAP (
        SB_in => SB_in,
        zero_fill_out => zero_fill_out
    );


    -- Stimulus process
    stim_proc: process

```

```
begin
    wait for 10ns;
    SB_in <= "110";
    wait;
end process;


END;
```



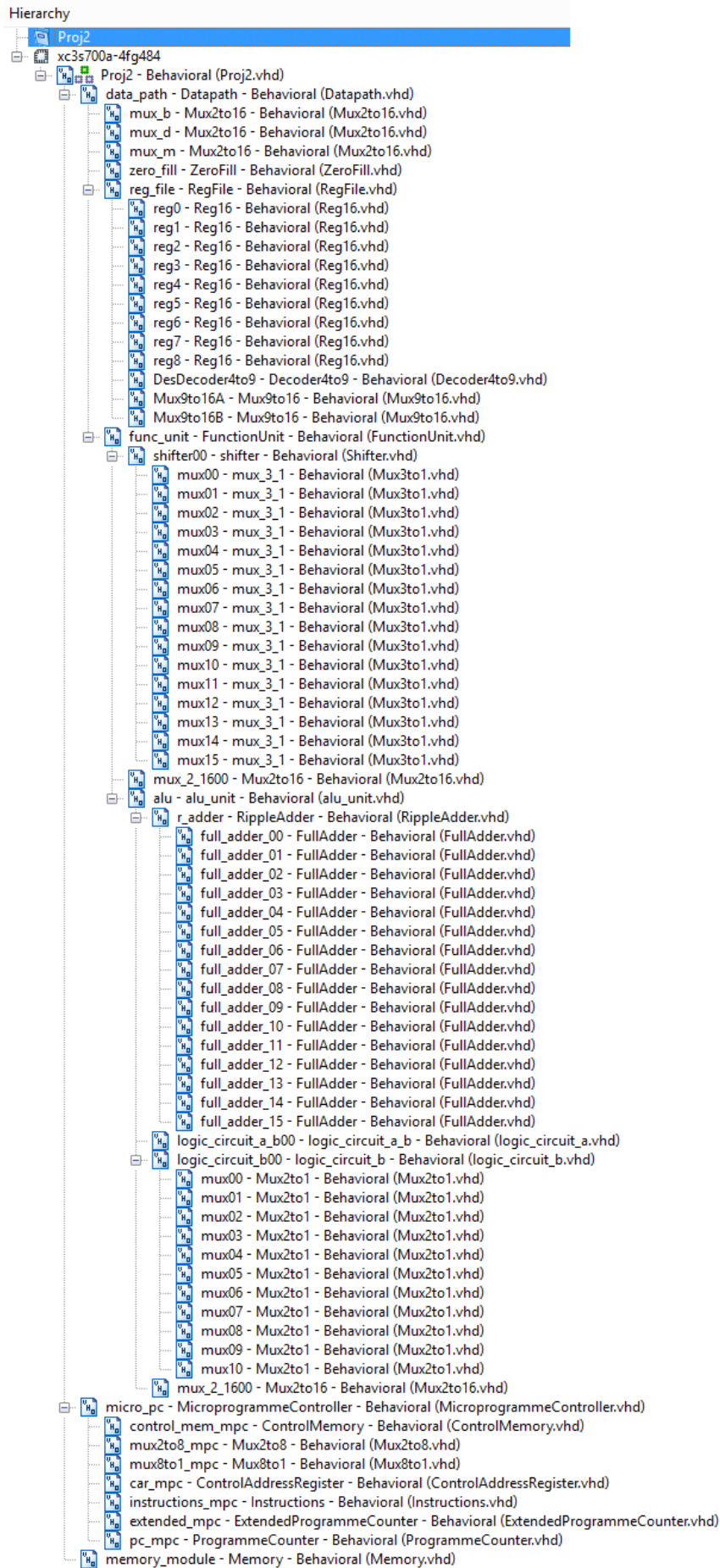





### 3.1 Control Address Register

 


### 3.2 Control Memory

 


### 3.3 Decoder 4-9 bit

 


### 3.4 Extended Programme Counter

 


## 3.5 Instruction Register

 


## 3.6 Memory Module

 


## 3.7 Mux 2-1 Bit

 


## 3.8 Mux 8-1 Bit

 


## 3.9 Mux 9-16 Bit

 



### 3.10 Programme Counter

 

### 3.11 Project 2 Top Level

 

### 3.12 Register File

 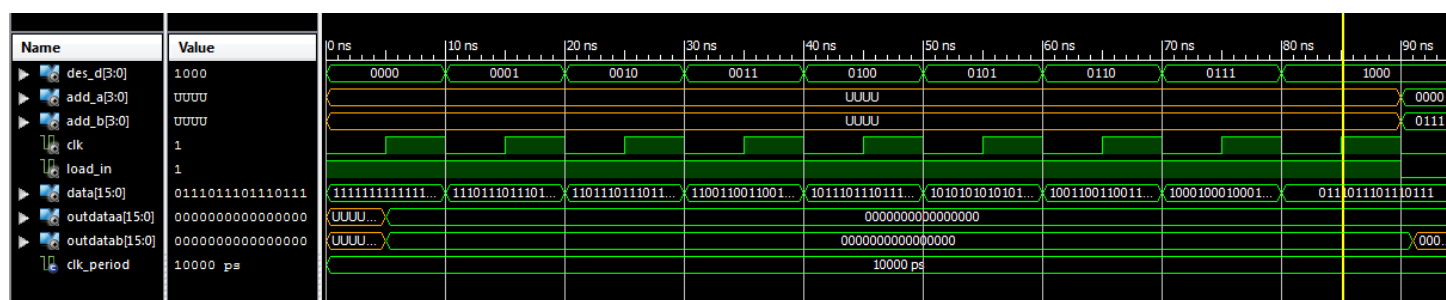

### 3.13 Zero Fill

